

# **Lecture 2: Electrical Components and Basic Circuits**

ME/AE 6705

Introduction to Mechatronics

Dr. Jonathan Rogers


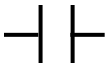
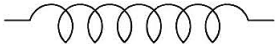




# Lesson Objectives

- Understand basic electrical components and circuit analysis methods
- Understand concept of resistance, capacitance, inductance, and impedance
- Understand op-amp circuits for amplification and input comparison
- Understand electrical switching elements including switches, relays, and transistors
- *Be able to design basic signal conditioning circuits*



# Basic Circuit Elements

Name	Reference Symbol	Circuit Symbol
Resistor	$R$	
Capacitor	$C$	
Inductor	$L$	
Ideal Voltage Source	$V$	
Ideal Current Source	$I$	

Constitutive Relationships:


$$V = IR$$



$$\frac{dV}{dt} = \frac{1}{C} I$$




$$\frac{dI}{dt} = \frac{1}{L} V$$

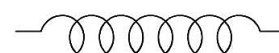

# Circuit Analysis

- Kirchhoff's Voltage Law
  - Sum of voltage drops and rises around any closed path in circuit is zero

$$\sum_{i=1}^N V_i = 0$$

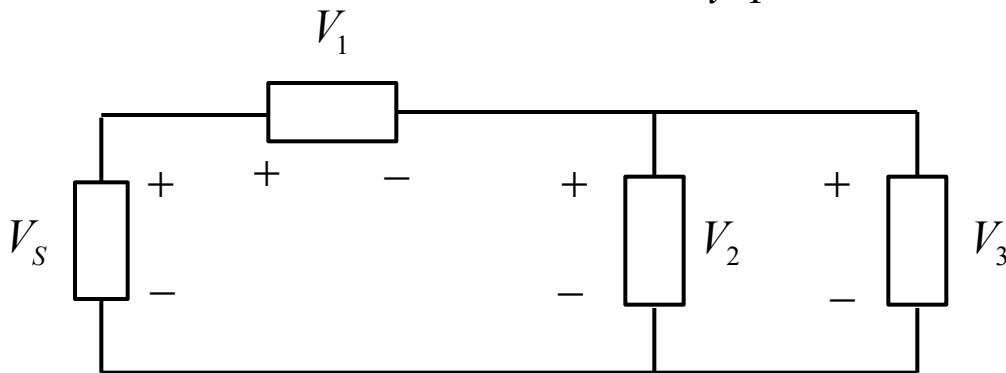

$$V_S - V_1 - V_2 = 0$$


$$V_S - V_1 - V_3 = 0$$



# Circuit Analysis

- Kirchhoff's Current Law
  - Sum of current into a node is zero

$$\sum_{i=1}^N I_i = 0$$

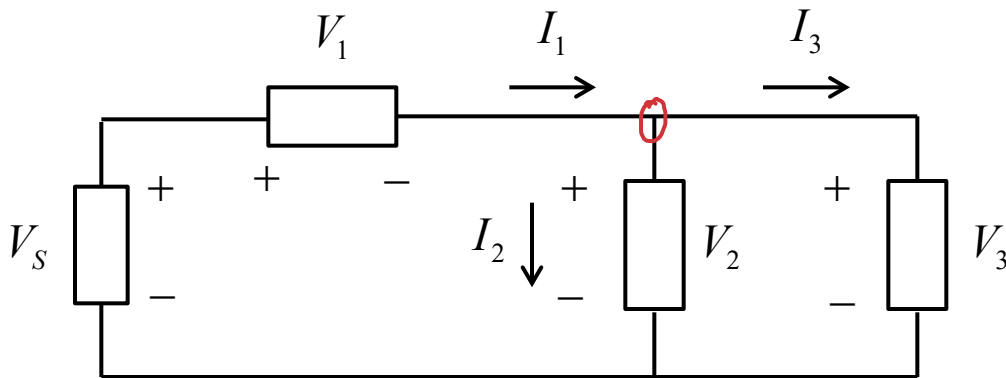


$$I_1 - I_2 - I_3 = 0$$


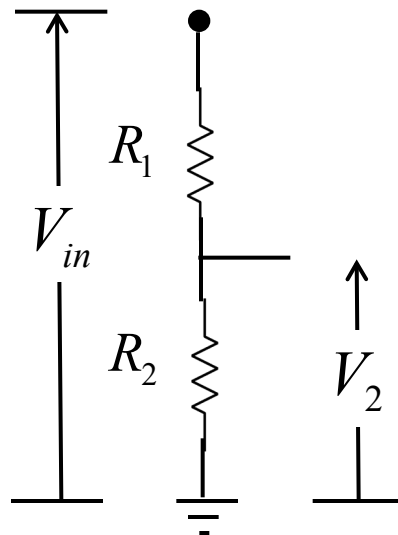
# Circuit Analysis

- By placing two resistors in series and taking voltage between resistors, we create a ***voltage divider***
  - Can be used to step down input source voltage for a sensor or processor (low-power applications)




$$V_2 = \frac{R_2}{R_1 + R_2} V_{in}$$

(derived using Kirchhoff's Laws)


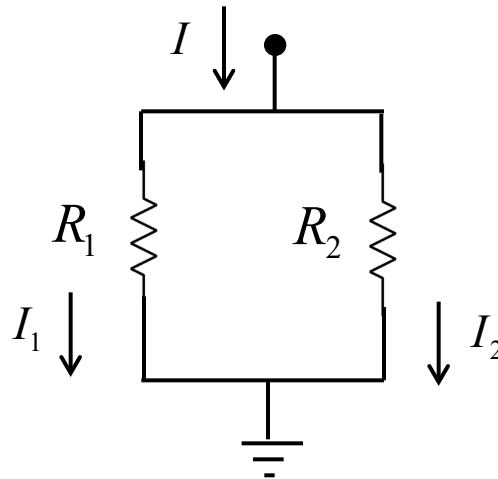
# Circuit Analysis

- By placing two resistors in parallel and taking current along one branch, we create a ***current divider***




$$I_2 = \frac{R_1}{R_1 + R_2} I$$

(derived using Kirchhoff's Laws)



# Example: Designing a Voltage Divider

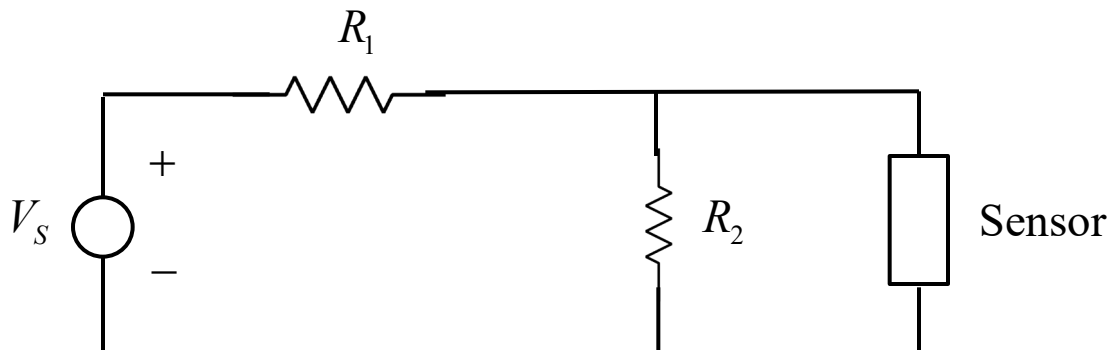- Problem: A certain sensor requires an input voltage of 5 VDC. You have a voltage source available which only provides 15 VDC. Design a voltage divider that will allow you to power the sensor from this power supply.



What are  $R_1$  and  $R_2$ ?

$$\frac{R_2}{R_1 + R_2} = \frac{1}{3}$$

$$\begin{aligned} R_2 &= 5 \text{ k}\Omega \\ R_1 &= 10 \text{ k}\Omega \end{aligned}$$





# Switch Types


- Switches defined as either **toggle** or **push-button**

## Toggle Switches


Single Pole,  
Single Throw  
(SPST)




Single Pole,  
Double Throw  
(SPDT)

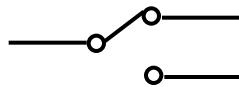

DPST

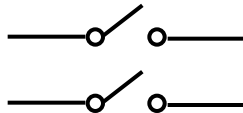


DPDT

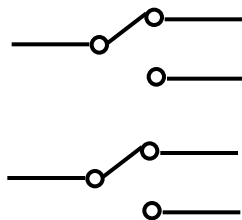


*pole* : # of separate circuits controlled  
*throw* : # of different positions / connections  
each pole can make

## Push-Button Switches

Normally Open  
(NO)

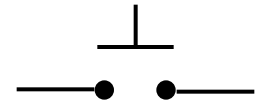


Normally Closed  
(NC)

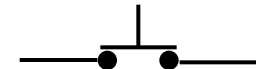

## Switch Bouncing Phenomenon

Requires use of  
debouncing circuit.

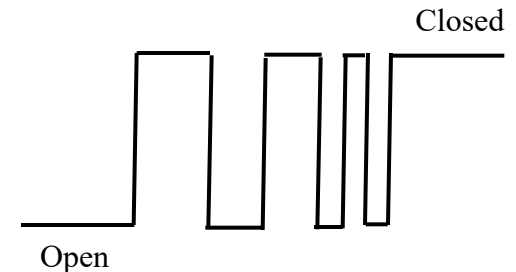


# AC vs DC Signals

- AC (alternating current) signals have sinusoidally varying voltage

$$V = V_0 \sin(\omega t + \theta)$$

$$\omega = 2\pi f = \frac{2\pi}{T}$$

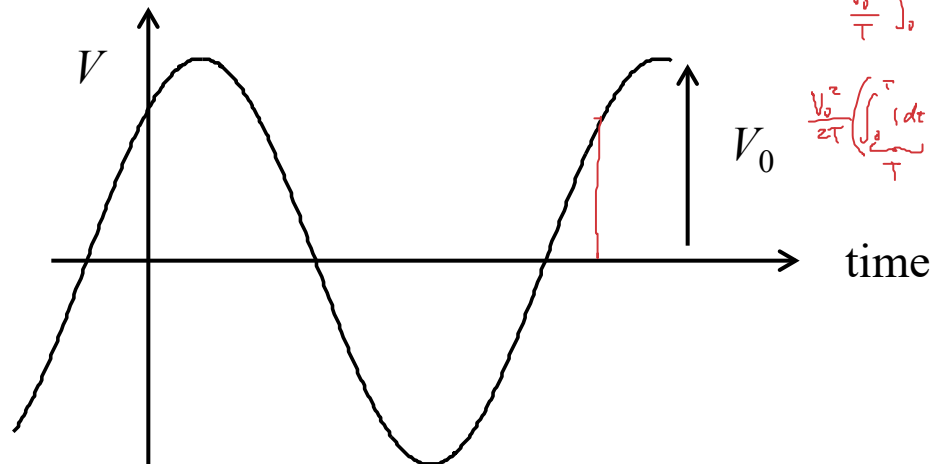DC Voltage occurs when voltage is constant with time ( $\omega = 0$ ).



$$\sin^2 x = \frac{1 - \cos 2x}{2}$$

$$\frac{1}{T} \int_0^T V^2 dt = \frac{1}{T} \int_0^T V_0^2 \sin^2(\omega t + \theta) dt$$

$$\frac{V_0^2}{T} \int_0^T \frac{1 - \cos(2\omega t + \theta)}{2} dt$$

$$\frac{V_0^2}{2T} \left( \underbrace{\int_0^T 1 dt}_T - \underbrace{\int_0^T \cos(2\omega t + \theta) dt}_{\text{integral over one period is 0}} \right)$$

↓

$$\frac{V_0^2}{2}$$

$$V_{RMS} = \sqrt{\frac{1}{2}} V_0 \approx 0.707$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V^2 dt} = 0.707 V_0$$

$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T I^2 dt} = 0.707 I_0$$

*Note: AC current from wall is 110 VAC, meaning the RMS voltage is 110 V.*

# Power

- Power defined as voltage times current

$$P(t) = I(t)V(t) \xrightarrow{\text{DC Voltage}} P = IV = I^2 R$$

$$\sin(A) \sin(B) = \frac{1}{2} [\cos(A-B) - \cos(A+B)]$$

AC Voltage



$$P(t) = V_0 I_0 \sin(\omega t + \theta_V) \sin(\omega t + \theta_I)$$

Instantaneous Power

$$P(t) = V_{RMS} I_{RMS} \underbrace{\cos(\theta_V - \theta_I)}$$

Average Power

adjust to bring closer to 0  
for more power

**Power factor:** Measures how much of supplied power is converted into real or useful power.




# Impedance

- Impedance ( $Z$ ) is generalization of resistance

$$Z = \frac{V}{I}$$

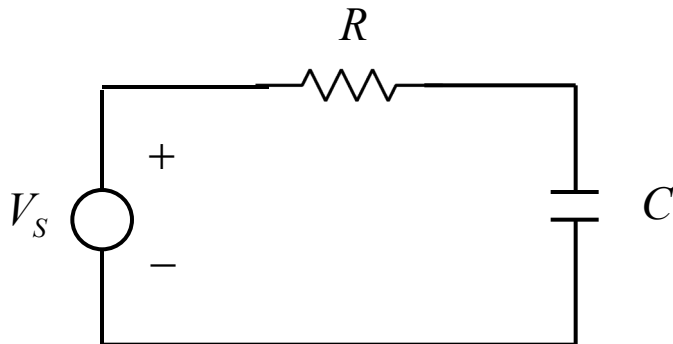- Basically gives us a measure of “resistance” in circuit that includes more elements than just resistors



RC circuit

Kirchhoff's Voltage Law:

$$V_s(t) = Ri(t) + \frac{1}{C} \int i(t) dt$$

$$V_s(s) = R i(s) + \frac{1}{C_s} i(s)$$

$$\frac{V_s(s)}{i(s)} = R + \frac{1}{C_s}$$

# Impedance

- Applying Laplace transform,

$$V_s(s) = Ri(s) + \frac{1}{Cs}i(s) \longrightarrow \frac{V_s(s)}{i(s)} = \underline{R + \frac{1}{Cs}}$$

If voltage varies sinusoidally with frequency  $\omega$ , can substitute  $s = j\omega$

$$\longrightarrow Z = \frac{V_s(j\omega)}{i(j\omega)} = R + \frac{1}{j\omega C}$$

↑  
Impedance due to capacitor


- For DC voltage source, **impedance of RC circuit is infinite**  $\omega = 0$
- For AC voltage source, **impedance of RC circuit approaches  $R$  as  $\omega \rightarrow \infty$**   $\text{high frequency : } Z \rightarrow R$

# Impedance

- Similar analysis for RL circuit yields:

$$Z = \frac{V_s(j\omega)}{i(j\omega)} = R + j\omega L$$

↑  
Impedance due to inductor

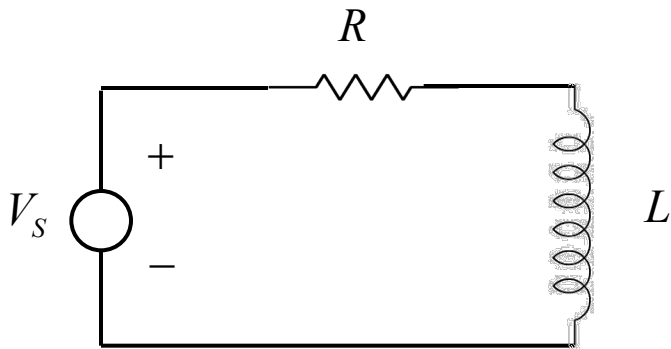

Impedance is an imaginary quantity:

$$Z = R + jX$$

$R = \text{resistance}$   
↑  
real part


$X = \text{reactance}$   
↑  
imaginary part  
Varies w/ frequency

What is impedance of a circuit with just a resistor load  $R_{total}$ ?

# Impedance: Practical Considerations


Ideal Voltmeter

Voltmeters have finite impedance

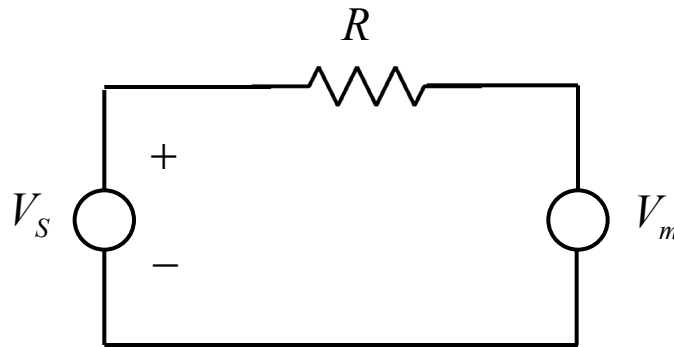

$$V_m = V_S$$


Actual Voltmeter  
(impedance  $R_m$ )

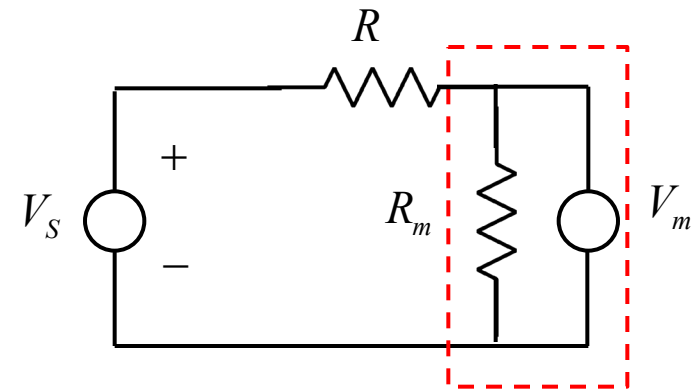

$$V_m = \frac{R_m}{R_m + R_S} V_S$$

- When connecting electrical devices together, important to make sure **impedances are matched**
- Otherwise high-impedance device can reflect back signal produced by low-impedance device
- **Impedance matching** can be accomplished by adding appropriate resistors to circuit

Function Generator  
(low impedance)

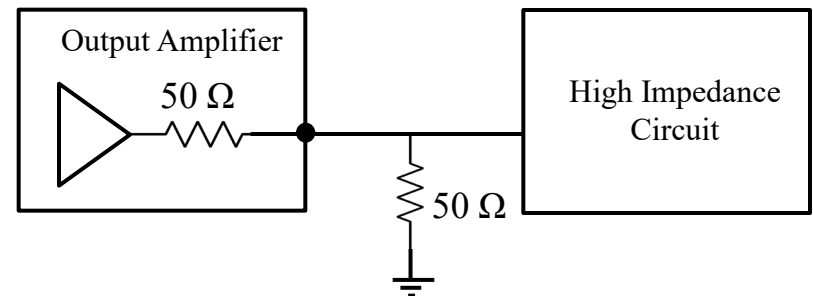

# Potentiometers

- Potentiometers and rheostats are variable resistors
  - Potentiometers have three terminals
  - Rheostats have two
- Useful for user interfaces, or to adjust resistor value to precise level needed in circuit design
  - Resistors only come in discrete values


Potentiometer Symbol



Potentiometer




Rheostat

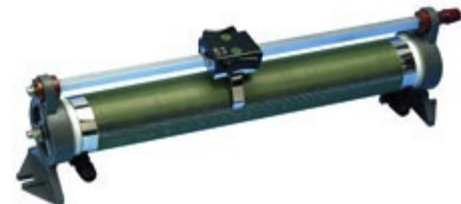



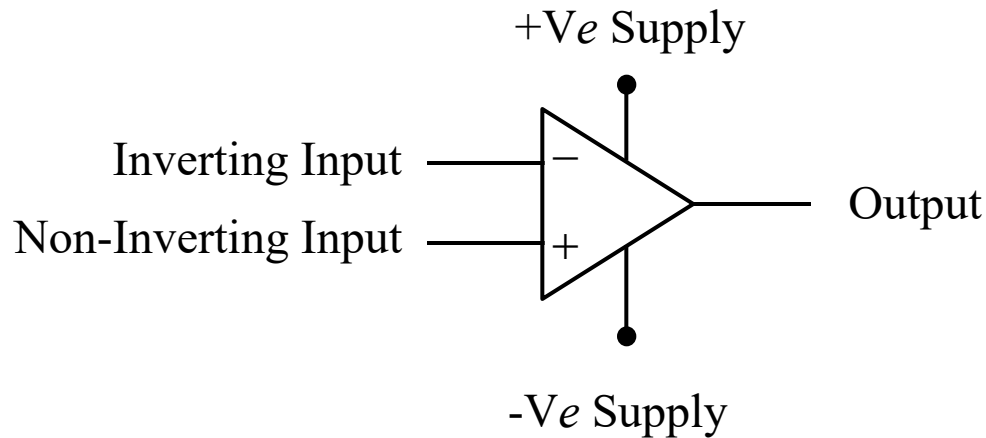
# Op-Amps

- Operational amplifiers are important circuit components
  - Used in signal amplification and other common circuits
  - Built from transistors, diodes, resistors, capacitors



# Op-Amps


- Open-loop operation of op-amps

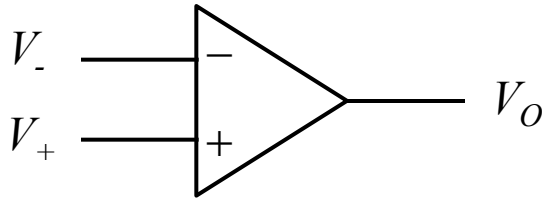

$V_O$  saturates at  $V_{sat}$  which is typically slightly smaller than supply voltage ( $\sim 13\text{V}$ )


$$V_O = K_{OL} (V_+ - V_-)$$

$$K_{OL} \approx 10^5 \text{ or } 10^6$$

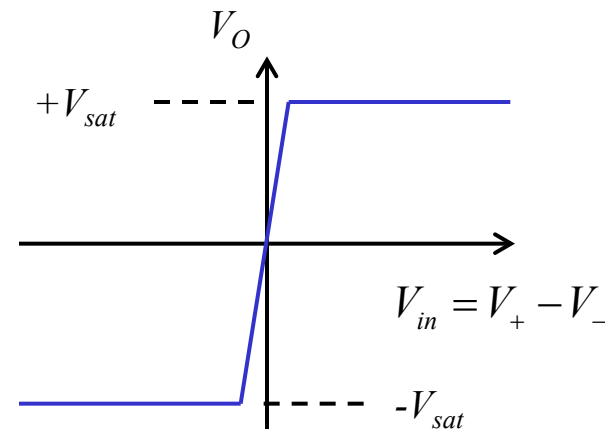
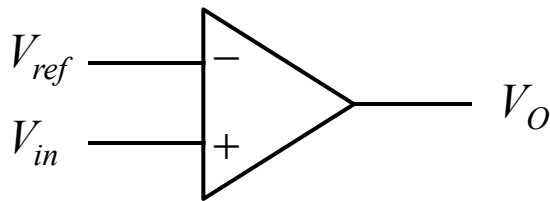
# Op-Amps

- Comparator Op-Amp Circuit
  - Useful application of open-loop op-amp
  - Used on-board microcontrollers
  - (Still requires supply voltage, although terminals not shown)



$$V_O = \begin{cases} +V_{sat} & \text{if } V_{in} > V_{ref} \\ -V_{sat} & \text{if } V_{in} < V_{ref} \end{cases}$$


Example use:

- Set output ON when sensor input exceeds certain threshold output.


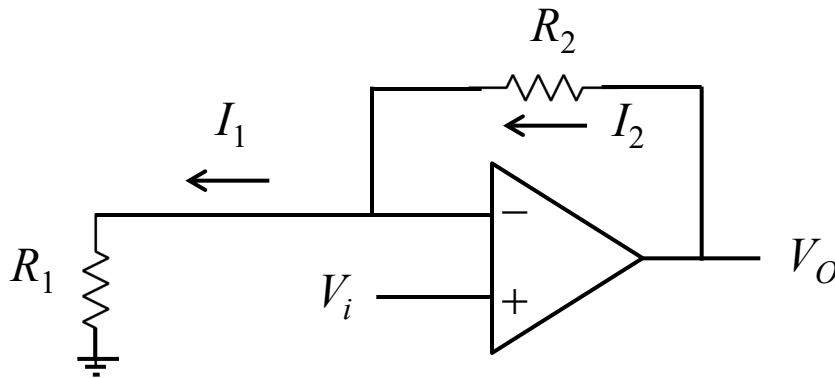
# Op-Amps

- Non-Inverting Op-Amp
  - Used to amplify voltage signal
  - For instance, signal conditioning for sensor




$$V_O = \frac{R_1 + R_2}{R_1} V_i = \left( 1 + \frac{R_2}{R_1} \right) V_i$$

- By sizing  $R_1$  and  $R_2$  appropriately, can amplify  $V_i$  to value we need at output  $V_O$
- Since resistors only come in discrete values, sometimes need to make  $R_1$  or  $R_2$  a potentiometer so it can be tuned to precise value we need.


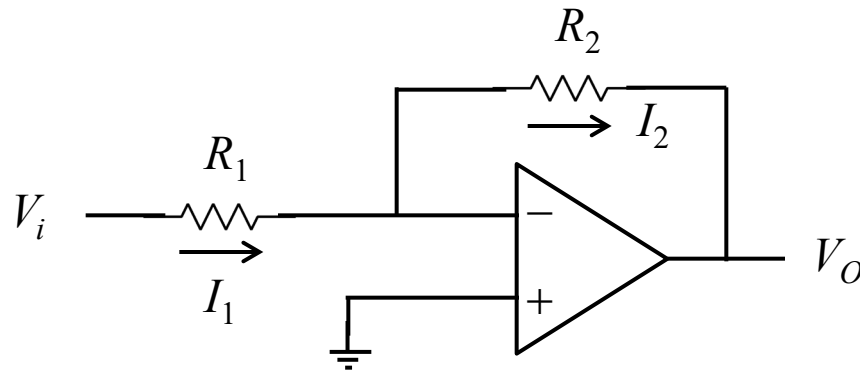
# Op-Amps

- Inverting Op-Amp
  - Used to amplify voltage signal and invert it
  - Also used in signal conditioning




$$V_O = -\frac{R_2}{R_1} V_i$$

- Again, by sizing  $R_1$  and  $R_2$  appropriately, can amplify  $V_i$  to value we need at output  $V_O$


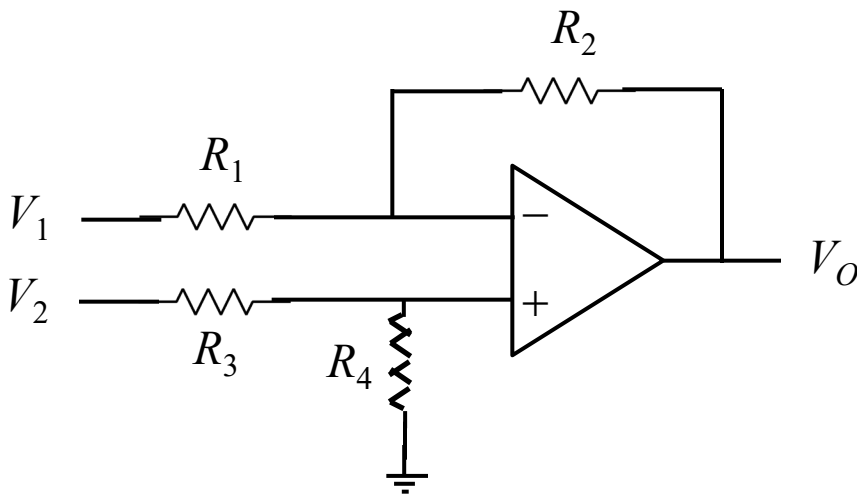
# Op-Amps

- Differential Op-Amp
  - Used to provide a measure of the difference between two voltage inputs



$$V_O = \frac{R_2}{R_1} (V_2 - V_1) = K_P (V_2 - V_1)$$

Example Use: Amplify difference between voltage outputs on arms of Wheatstone bridge used to measure strain.



# Example: Signal Amplification

- Using an op-amp, design a circuit that takes an input voltage  $V_i$  and produces an output voltage  $V_o = kV_i$  which is tunable from  $1 \leq k \leq 10$ . Determine the circuit components needed and an expression for the value of  $k$ .

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$

$$0 \leq \frac{R_2}{R_1} \leq 9$$


$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = [0, 9] \text{ k}\Omega \quad \text{potentiometer}$$


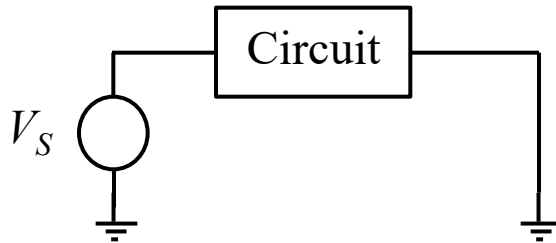
# Grounding

- Ground loops can cause serious problems (bias and noise) in circuit design
  - Must make sure that all ground points are connected to same ground (**common ground**)
  - Connections to multiple different grounds can cause feedback current between grounds




*Bad idea...these grounds may be at different electrical potentials.*




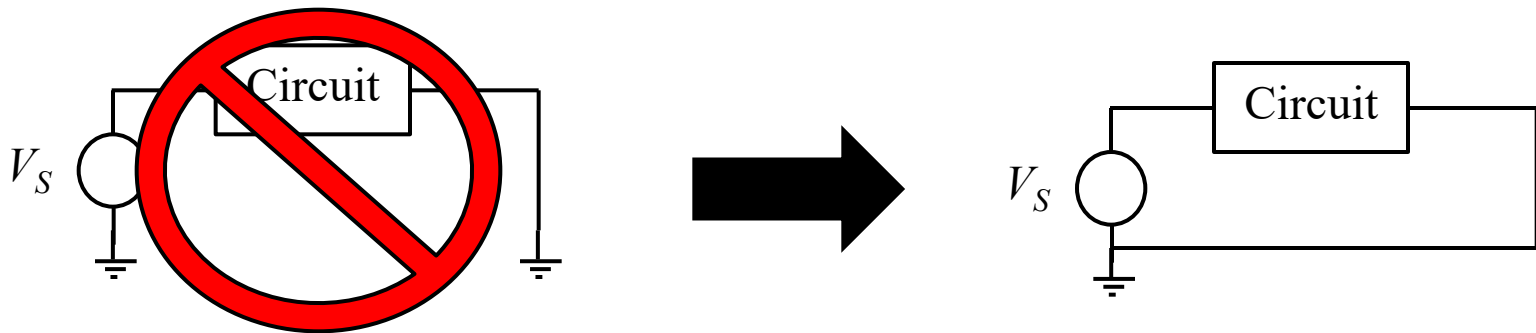
# Grounding

- Ground loops can cause serious problems (bias and noise) in circuit design
  - Must make sure that all ground points are connected to same ground (**common ground**)
  - Connections to multiple different grounds can cause feedback current between grounds



# Semiconductors



- Semiconductors are special materials that are between conductors and insulators
- They can be made to conduct current if sufficient voltage is present
- Most important semiconductor device is the transistor, which can be viewed as a solid-state switching device
  - Logic gates
  - Interface between processors and mechanical devices





# Diodes

- Diodes are semiconductor devices that only allow current to flow one way

Symbol

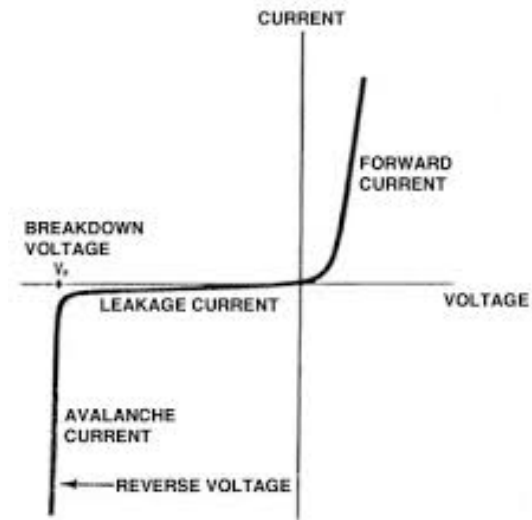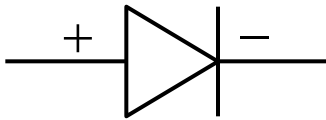


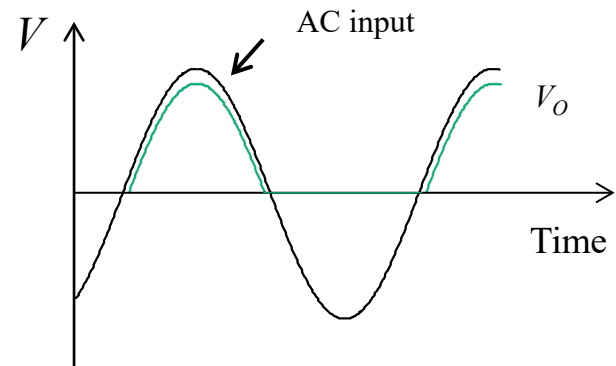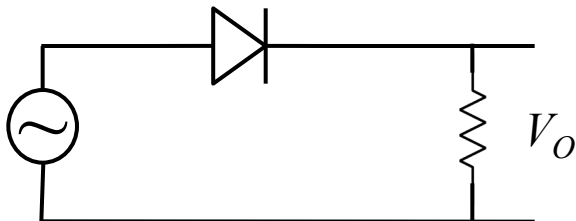Example Use: Rectify AC voltage into DC voltage.


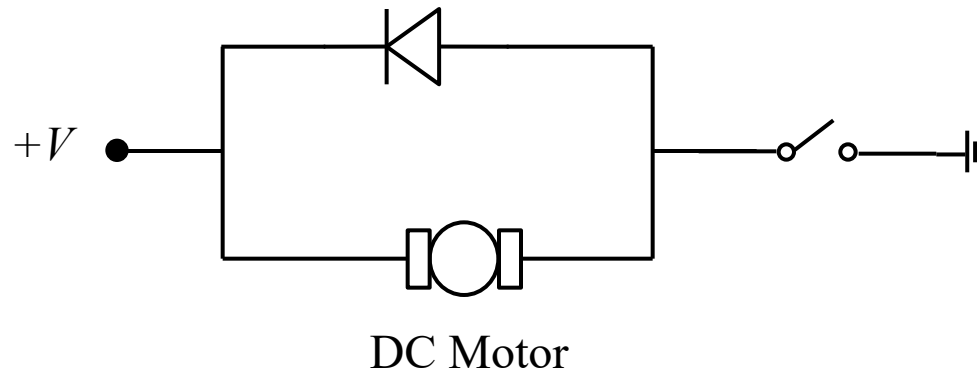
# Flyback Diodes

- Consider following circuit for motor control using switch




- Motor has high inductance  $L$
- When motor switched off, voltage develops across motor terminals according to:

$$V = L \frac{di(t)}{dt}$$


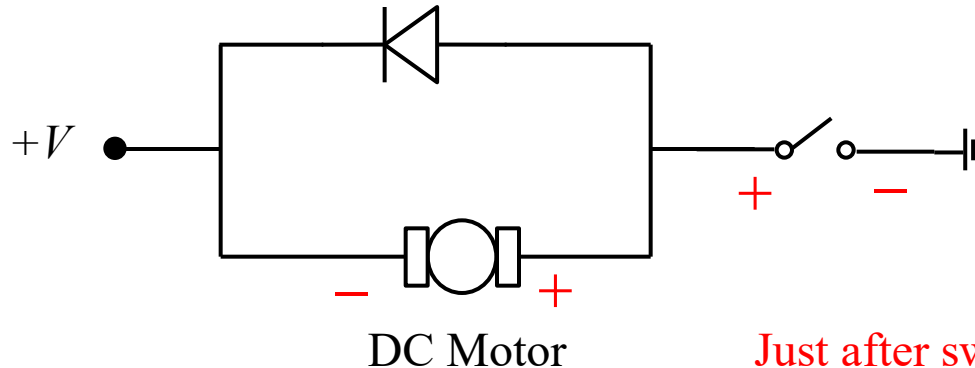
# Flyback Diodes

- Consider following circuit for motor control using mechanical switch



Just after switch closing...

$$\text{as } i(t) \rightarrow 0 \\ \frac{di(t)}{dt} \rightarrow \text{large negative value}$$

$$V = L \frac{di(t)}{dt}$$


- High voltage of opposite polarity across switch terminals just after closing
- May cause wear on switch due to arcing, or may blow out transistor
- Flyback diode provides an alternative path for current in motor coil and mitigates arcing**



# LED's and Photodiodes

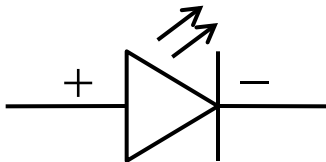
## Light Emitting Diodes

- Emit light when “forward biased”
- Have voltage drop of about 2V when on
- Colors determined either by semiconductor material or plastic housing over diode



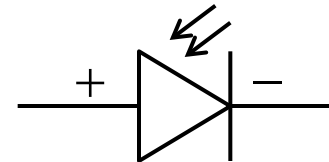
## Photodiodes

- Opposite of LED
- Amount of current diode passes is proportional to amount of light it receives
- Commonly used as light sensors (i.e., nightlight)


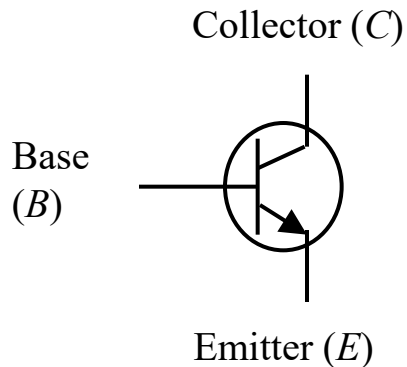
# BJT Transistors

- Bipolar Junction Transistors (BJT's) are common circuit elements used primarily for switching
- Idea is that we can switch a current path on or off by activating a second “base” path



- BJT is current controlled device where amount of current supplied at  $B$  determines current flow from  $C$  to  $E$
- Small base current allows much larger current to flow from collector to emitter
- Two important states: Off, and Saturation State
- Voltage at emitter ( $V_E$ ) always lower than voltage at base ( $V_B$ ) by about 0.6V
- Must always have  $V_C > V_E$

$$V_{BE} = V_B - V_E$$


$$V_{CE} = V_C - V_E$$



# BJT Transistors
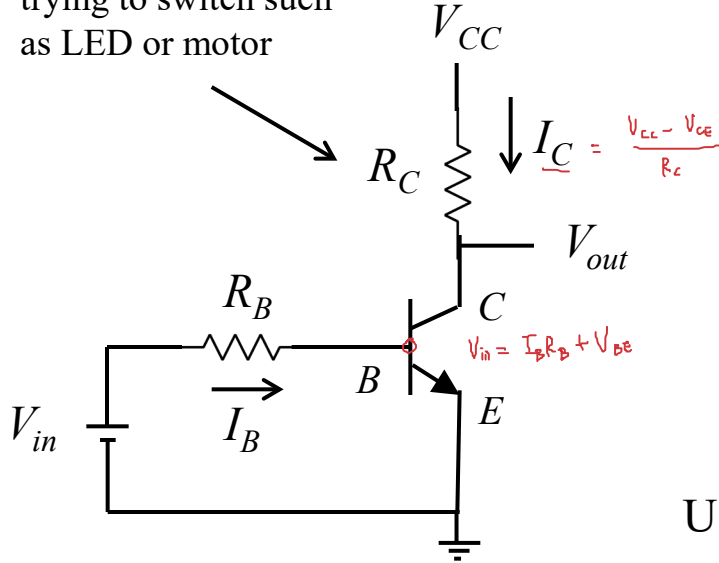
## • Transistor Switch Circuit

Can be load we are trying to switch such as LED or motor



- Suppose we want to control current flow  $I_C$  using input voltage  $V_{in}$
- When  $V_{in} = 0$ , no current flows between collector and emitter and thus  $I_C = 0$  (and  $V_{out} = V_{CC}$ )
- Question: What voltage  $V_{in}$  is required to switch transistor from off state to saturation state (allowing current to flow through load)?

Use KVL:  $V_{in} = I_B R_B + V_{BE}$

Use KCL:  $I_C = (V_{CC} - V_{CE}) / R_C$

Property of BJT's just before saturation:


$$I_B = I_C / \beta \quad (\beta \approx 100)$$

Equations can be solved to determine  $V_{in}$


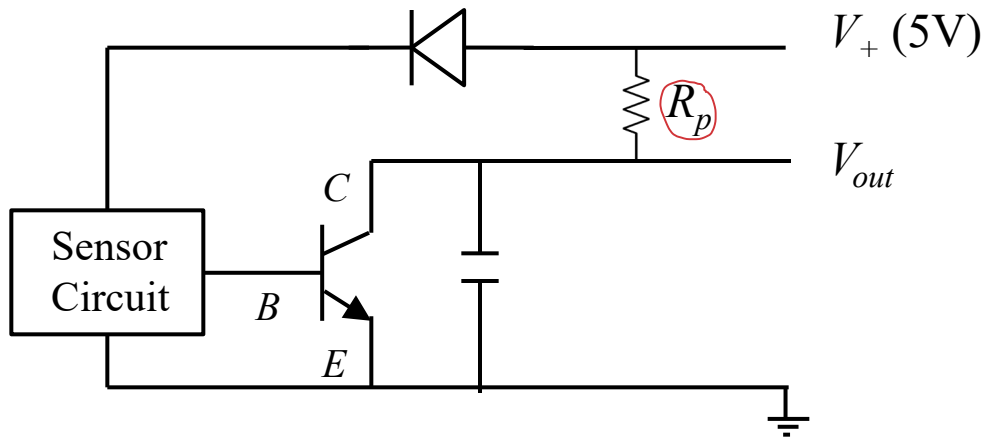
# BJT Transistors

- Open Collector Output
  - Used often to take sensor output and convert to digital high (5V) or low (0)



- Output of sensor drives base of transistor
- $R_p$  is “pull-up” resistor connected from reference voltage  $V_+$  to output  $V_{out}$
- When sensor is low, transistor is in OFF state and no current flows from  $C$  to  $E \rightarrow V_{out} = 5V$
- When sensor is high, transistor is in saturation and current flows from  $C$  to  $E \rightarrow V_{out} \approx 0$

# BJT Transistors


- Common specifications (found in component datasheet)

Part #	Max $V_{CE}$	Max $V_{BE}$	Max $I_C$	Power Dissipation at 25 deg C
2N3904	40 V	6 V	200 mA	0.625 W
TIP29	40 V	6 V	1 A	30 W
TIP102	100 V	5 V	8 A	80 W


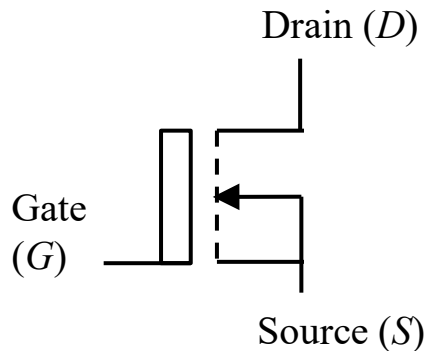
# MOSFET Transistors

- Metal-Oxide Semiconductor Field Effect Transistors (MOSFET's) are another type of transistor commonly used for switching
- Unlike BJT's, MOSFET's use voltage as switching signal rather than current



- MOSFET is voltage controlled device where voltage supplied at  $G$  determines current flow from (or resistance between)  $D$  to  $S$
- Two important states: Off and Saturation State
- When transistor is off, drain-source resistance is very high  $\rightarrow$  no current flows from  $D$  to  $S$
- When transistor is ON, drain-source resistance is very low ( $< 1 \Omega$ ) and current flows from  $D$  to  $S$
- Internal resistance at gate is very high ( $10^{14} \Omega$ ) – thus no current flows into gate (gate circuit “separate” from drain-source circuit)


# MOSFET Transistors

- Some other important values/considerations

$V_{GS}$  : Gate-source voltage

$V_{GS(th)}$  : Threshold gate-source voltage. If  $V_{GS} < V_{GS(th)}$  transistor is in OFF state. If  $V_{GS}$  is significantly higher than  $V_{GS(th)}$ , transistor is in ON (saturation) state.

$V_{DS}$  : Drain-source voltage

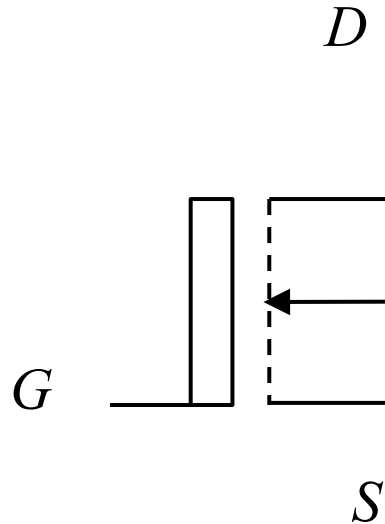

*Thus, like BJT,  
MOSFET acts as a  
solid-state switch.  
Switching times are  
usually in the  
nanosecond range.*



# MOSFET Transistors

Part #	On Resistance $R_{DS(on)}$	Max Current Drain $I_{D(max)}$	Power Dissipation $P_D$	Gate Threshold Voltage $V_{GS(th)}$	Drain-to-Source Breakdown Voltage $V_{dss}$	Type
2N4351	$\leq 300 \Omega$	100 mA	375 mW	1-5 V	$\geq 25 V$	Logic-level MOSFET
NTE2980	0.2-0.28 $\Omega$	6.7 A	25 W	1-2 V	$\geq 60 V$	Normal MOSFET
IRFZ14	0.2 $\Omega$	10 A	43 W	2-4 V	$\geq 60 V$	Power MOSFET

$R_{DS(on)}$  : Resistance between drain and source terminals when MOSFET is fully on.


$I_{D(max)}$  : Max current that can be passed between drain and source.

$V_{dss}$  : Maximum voltage between drain and source when transistor is off. If voltage between  $D$  and  $S$  exceeds this value when in OFF state, current will start to flow.

# MOSFET Transistors

- MOSFETs commonly used for switching to drive motors or LEDs


## MOSFET Circuit for Driving a Motor

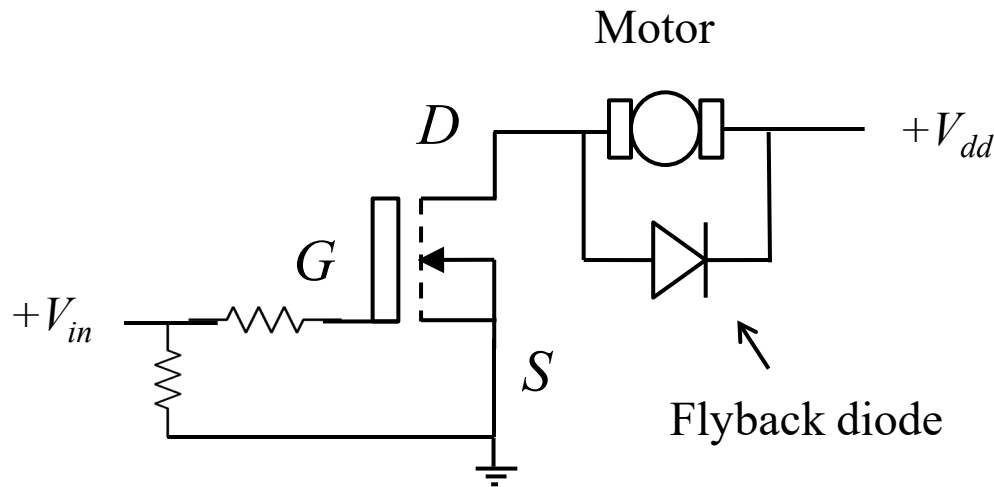

- When  $V_{in}$  is below threshold voltage, transistor is OFF and no current flows through motor
- When  $V_{in}$  is well above threshold voltage, transistor is ON and current flows through motor
- Flyback diode protects MOSFET from large voltage buildup when transistor is switched from on to off
- Resistor used to ground gate terminal when  $V_{in} = 0$  to turn transistor completely off
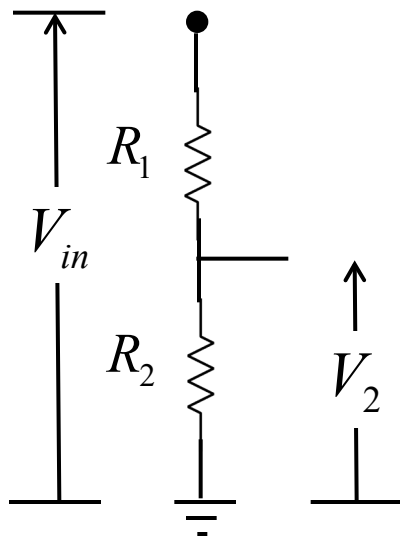
# Reducing Voltage Levels

- Recall voltage dividers
  - Can be used to step down voltages for low-power applications
  - *Should never use a voltage divider to supply power to a load*
  - Only for use in low-current applications with high values of  $R_1$  and  $R_2$  (in the 1 k $\Omega$  - 10 k $\Omega$  range)




- While providing power, current will flow through  $R_1$  and  $R_2$
- This means resistors will dissipate power in the form of heat
- If any substantial current flows through voltage divider, it *generates excessive heat* and is *power inefficient*



# Voltage Regulators


- Voltage regulators are semi-conductor devices that provide very efficient, stable mechanism for stepping down voltages
  - Will provide single output voltage (e.g., 5V) for a range of input voltages (e.g., 7-35V)

## Linear Voltage Regulator

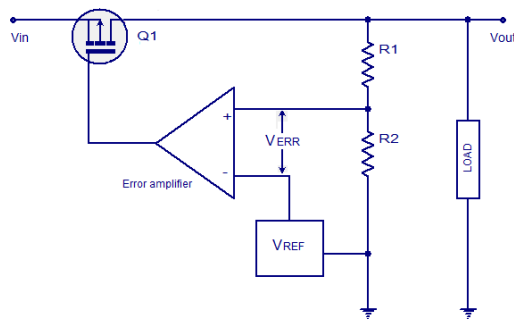

*Uses differential amplifier and transistor to achieve stable output voltage*

## Switching Voltage Regulator

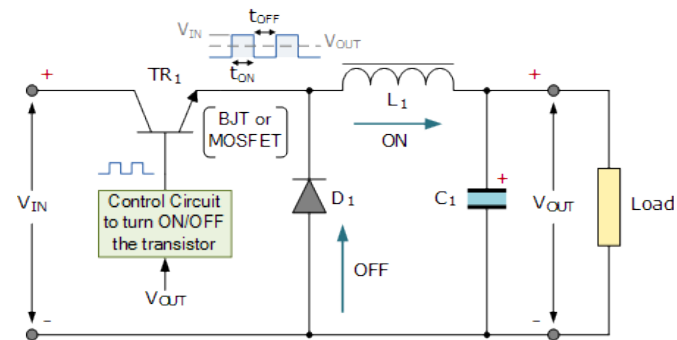


*Switches gate / base of transistor at specific rate to achieve stable output voltage*



# Voltage Regulators

- Common linear voltage regulator: 7805

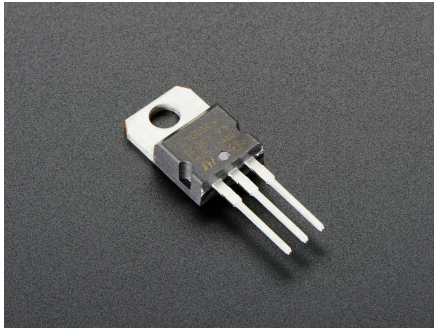

- Output voltage: 5 V
- Input voltage range: 7-35V
- Maximum current provided: 1.5A
- Dropout voltage: 2V
- Cost: \$0.75

- All linear regulators have a dropout voltage
  - This describes how much higher input voltage must be than desired output voltage
- Heat dissipation is an issue – regulators must be attached to heat sink for high power applications


$$P = (V_I - V_O)I$$

*Power dissipation equation for regulator*

# H-Bridge Drives

- Commonly used to drive motors in both directions
  - Typically used to drive brushless and brushed DC motors
  - Critical element in servo drives

*Typical Hobby  
Servo*

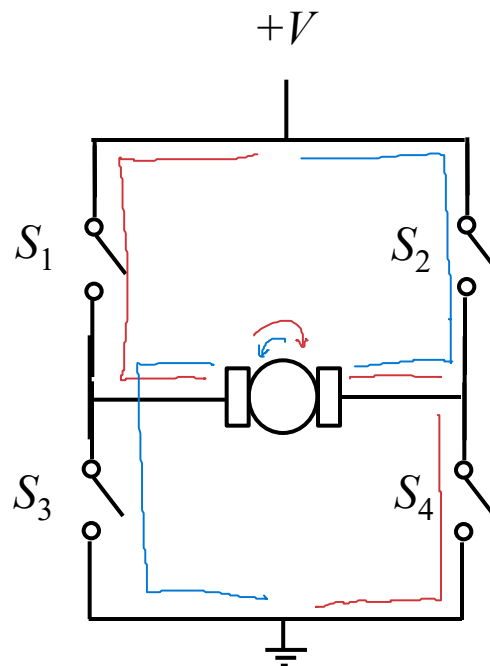


## Simple H-Bridge Schematic

- When switches  $S_1$  and  $S_3$  are open and  $S_2$  and  $S_4$  are closed, motor turns one direction
- When switches  $S_1$  and  $S_3$  are closed and  $S_2$  and  $S_4$  are open, motor turns other direction


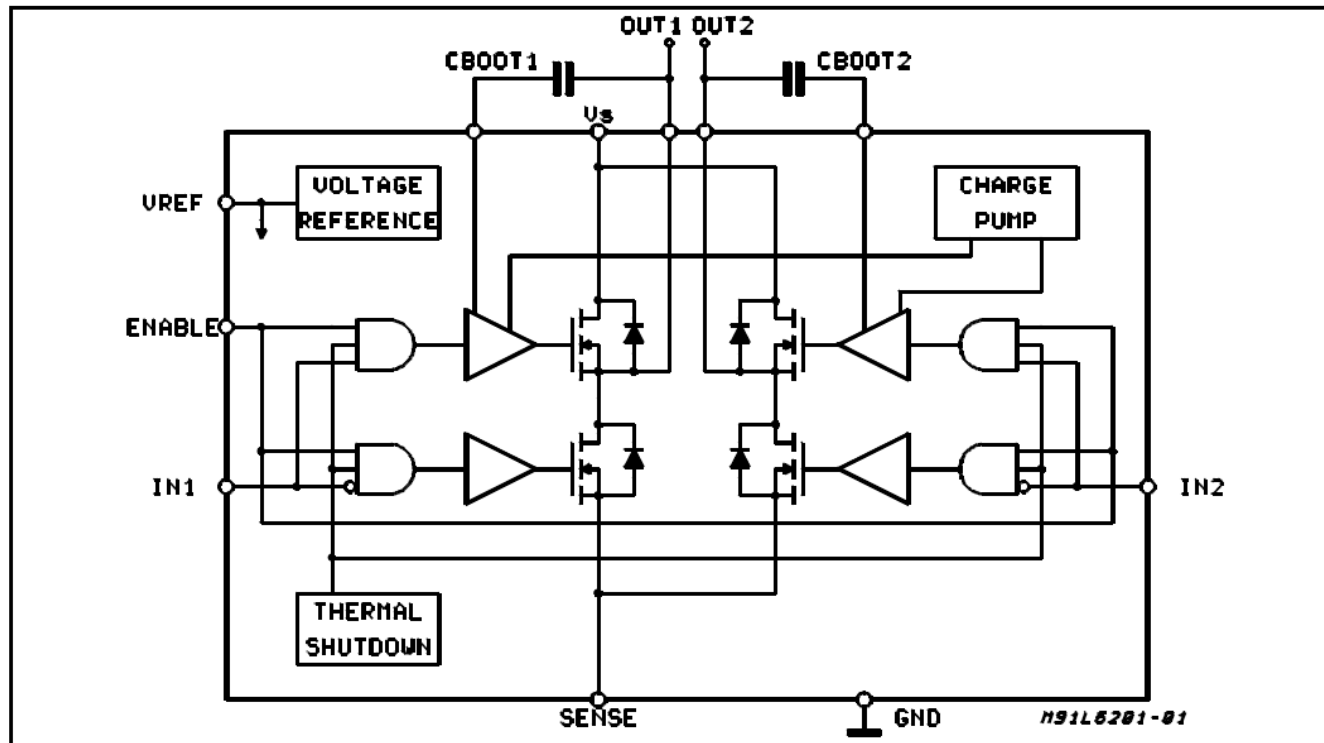
# H-Bridge Drives

- H-Bridges are built from transistors, diodes, and logic gates
  - Yields very fast switching times



STMicro L6203  
H-bridge

*Note flyback diodes incorporated next to MOSFETs. Motor connects across two output terminals.*



# Example: Op-Amp Signal Conditioning

- Consider the signal conditioning op-amp circuit shown below, with an ideal diode in the feedback loop. Derive the input-output ratio  $V_O/V_i$  for the case when  $V_O < 0$  and  $V_i > 0$ .

*ideal diode : no voltage drop ?*

$$R_{23} = \frac{R_2 \cdot R_3}{R_2 + R_3}$$

$$\frac{V_O}{V_i} = - \frac{R_2 R_3}{R_1 (R_2 + R_3)}$$

